



Výstupy

A	B	C	D	E	F
x	y	z	z	y	x

Zakódování

vstupy

I	x_1	x_2
I_3	0	0
I_2	0	1
I_1	1	0
-	1	1

výstupy

Y	Y_1	Y_2
x	0	0
y	0	1
z	1	0
-	1	1

stavy

S	S_1	S_2	S_3
A	0	0	0
B	0	0	1
C	0	1	0
D	0	1	1
E	1	0	0
F	1	0	1
-	1	1	0
-	1	1	1

D-klopný obvod

Q_N	D	Q_{N+1}
0	0	0
0	1	1
1	0	0
1	1	1